

Question -1

a. Thermal voltage calculation

To find the thermal voltage (V_T) at 25°C , we use the formula:

$$V_T = \frac{kT}{q}$$

Temperature (T): $25^\circ\text{C} + 273 = 298\text{K}$

Boltzmann's constant (k): $1.38 \times 10^{-23} \text{ J/K}$

Charge of an electron (q): $1.602 \times 10^{-19} \text{ C}$

Substituting the values:

$$V_T = \frac{(1.38 \times 10^{-23} \text{ J/K})(298\text{K})}{1.602 \times 10^{-19} \text{ C}} \approx 25.69 \text{ mV}$$

b. Diode Current calculation

Using the ID equation provided:

$$I_D = I_S (e^{V_D/nV_T} - 1)$$

Saturation current (I_S): $40 \text{ nA} = 40 \times 10^{-9} \text{ A}$

Ideality factor (n): 2

Applied voltage (V_D): 0.5 V

Thermal voltage (V_T): 0.02569 V

$$I_D = 40 \times 10^{-9} \cdot (e^{0.5/(2 \cdot 0.02569)} - 1)$$

$$I_D = 40 \times 10^{-9} \cdot (e^{9.7314} - 1)$$

$$I_D = 40 \times 10^{-9} \cdot (16837.2) \approx 0.673 \text{ mA}$$

Question 2

Ⓐ Approximate Model ($V_D = 0.7V$)

$$V_D : 0.7V$$

$$V_R : E - V_D = 30V - 0.7V = 29.3V$$

$$I_D : V_R / R = 29.3V / 1.5k\Omega = 19.53mA$$

Ⓑ Ideal Model ($V_D = 0V$)

$$V_D : 0V$$

$$V_R : E - V_D = 30V - 0V = 30V$$

$$I_D : V_R / R = 30V / 1.5k\Omega = 20mA$$

Ⓒ Yes, the ideal model provides a good approximation in this case. The difference in current is only about 2.4%. This is because the source voltage (30V) is significantly larger than the diode's forward voltage drop (0.7V).

Question 3

Ⓐ Reverse Bias Case:

The battery is oriented with the negative terminal facing the diode's anode. Since the anode is at a lower potential than the cathode the diode is of

$$I = 0 \text{ A}$$

Ⓑ The 20V source is oriented such that the node connecting the diodes is at -20V relative to ground. Both diodes are Forward Biased because their anodes are grounded (higher potential) and cathodes are at -20V.

$$I_1 (10\Omega) : (20\text{V} - 0.7\text{V}) / 10\Omega = 1.93 \text{ A}$$

$$I_2 (20\Omega) : (20\text{V} - 0.7\text{V}) / 20\Omega = 0.965 \text{ A}$$

$$\text{Total } I : 1.93 \text{ A} + 0.965 \text{ A} = 2.895 \text{ A}$$

Ⓒ Back-to-Back series case

The middle branch contains two Si diodes in series but they are oriented opposing each other. This creates an open circuit for the middle branch. The current flows through the 10Ω resistor branch only.

$$I = 10\text{V} / 10\Omega = 1 \text{ A}$$

Question 4

① Si and GaAs in parallel

Source : 1V

Diodes : Si (0.7V) and GaAs (1.2V) in parallel

$$V_o = 1V - 0.7V = 0.3V$$

$$I = V_o / R = 0.3V / 1k\Omega = 0.3mA$$

② Multi-stage Si Network

path : From +16V through one Si diode, then

through a parallel pair of Si diodes, to the output V_o

③ Total diode voltage drop = $0.7V + 0.7V = 1.4V$

$$V_o : 16V - 1.4V = 14.6V$$

$$I = (V_o - (-4V)) / 4.7k\Omega$$

$$= (14.6 + 4) / 4.7k\Omega$$

$$= 18.6 / 4.7k\Omega$$

$$\approx 3.96mA$$